

Resistance Temperature Detectors



Dr. Christopher M. Godfrey
University of North Carolina at Asheville

ATMS 320

http://www.ncsu.edu/ncsu/comp/comp/edu/edu/ATMS_320/ATMS_320.html

Resistance temperature detectors (RTDs) are often made of platinum

- Why platinum?
 - Stable element
 - Resists corrosion
 - Easily workable
 - High melting point
 - Easily purified



Source: <http://www.diamond-studio.co.uk/jewelryshop/>



Source: <http://www.campbellsci.com/pt100>

ATMS 320


Platinum RTD Transfer Equation

- R_0 = Resistance at T_0 (usually, $T_0 = 0^\circ\text{C}$)
- a = first-order temperature coefficient
- b = second-order temperature coefficient
- R_T = resistance of the sensor at temperature T
- For a typical platinum RTD:
 - $a = 3.85 \times 10^{-3} \text{ }^\circ\text{C}^{-1}$
 - $b = -5.85 \times 10^{-7} \text{ }^\circ\text{C}^{-2}$

ATMS 320

121

A simple platinum RTD application:
Voltage divider

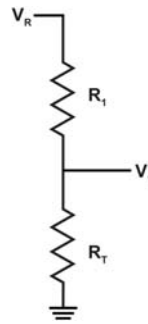


ATMS 320

122

A better platinum RTD application:
Bridge circuit

Let: $R_0 = R_T$ at 0°C
 $V_R = 5 \text{ V}$
Then at 0°C , $V_3 = 0 \text{ V}$

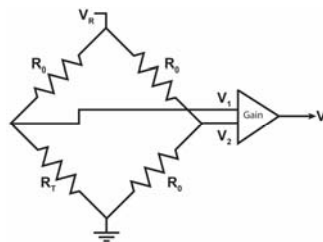


ATMS 320

123


ATMS 320

A better platinum RTD application: Bridge circuit

Now assume that 50°C is the maximum temperature that we care to measure in the field...

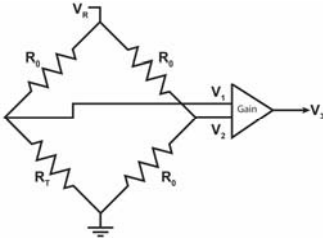

ATMS 320

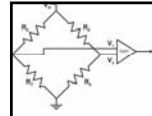

ATMS 320

A better platinum RTD application: Bridge circuit

Say we want the output of the sensor at the maximum temperature (50°C) to be 5 V. Since we know that the input is 5 V, the required gain is therefore _____.


ATMS 320

A better platinum RTD application: Bridge circuit



For a 0±5 V system, we now use the entire span!

ATMS 320

Why use a bridge circuit?

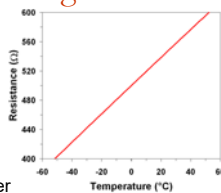

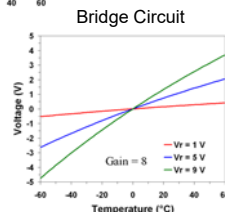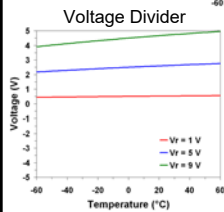Resistance vs. Temperature for a Platinum RTD



Static sensitivity of a platinum RTD in a bridge circuit

Uh-oh...Don't resistors dissipate heat?

- If we pass a current through a conductor with non-zero resistance, the conductor will consume power and dissipate heat
- The resulting “self-heating” of the sensor will cause an error
- The self-heating specification (in terms of power per degree C) describes the relationship between this temperature increase and the power dissipation for a given transducer

ATMS 320

Power dissipated by an RTD

ATMS 320

Power dissipated by an RTD

- Say we have a sensor with a self-heating specification of $4 \text{ mW } ^\circ\text{C}^{-1}$ and we are willing to tolerate a maximum self-heating error of 0.1°C
 - Must limit current flow to avoid exceeding tolerable error
 - This sets an upper limit on V_R

ATMS 320

How to select the gain and input voltage

- Since we are limited by the self-heating specification and self-heating error to a power dissipation of 0.4 mW , we must now determine the maximum allowable input voltage
- This ensures that the current through the bridge circuit is low enough to avoid exceeding the maximum allowable power dissipation
- For $R_T = R_0 = 500 \Omega$,

ATMS 320

How to select the gain and input voltage


- Now calculate the necessary gain so that V_3 is as close as possible to 5 V for our bridge circuit example:

A gain of _____ is necessary, given the required maximum input voltage, so that the output is 5 V at 50°C .

ATMS 320

How are RTDs typically made?

- Wrap a fine wire (e.g., platinum) around a substrate (a substrate is some supporting material on which a circuit is formed or fabricated)
- Cut the wire to the appropriate length to create a precisely known resistance at $T = 0^\circ\text{C}$
- Since the wire is very fragile, the form must be chosen such that it has a small β (e.g., glass)
- Another method is to etch the wire path onto a small circuit board

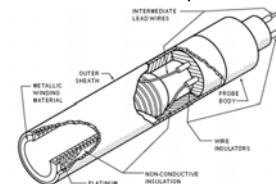

Source: H01 (www.rftcorp.com/learn/learn.php?c=01) © 2008

ATMS 320

RTD Advantages

- Low resistance: 100 Ω (most common) to 1000 Ω
- High sensitivity compared with thermocouples
- Very accurate ($\pm 0.0006^\circ\text{C}$ to 0.1°C)
- Nearly linear over a wide temperature range (more so than thermocouples)
- Wide span of operating temperatures (-200°C to 850°C)
- Operates in high temperatures
- High repeatability and stability
 - Low drift (industrial models drift $< 0.1^\circ\text{C year}^{-1}$)
 - Precision RTDs may drift only $0.0025^\circ\text{C year}^{-1}$

ATMS 320

RTD Disadvantages

- Fairly expensive (they're made of platinum!)
- Low static sensitivity
- Requires excitation and supporting circuitry
- Fragile wire (sensitive to shock and vibration)
- Low absolute resistance (i.e., resistance of long lead wires can affect sensor accuracy)
- Self-heating error
- Slow response time

ATMS 320